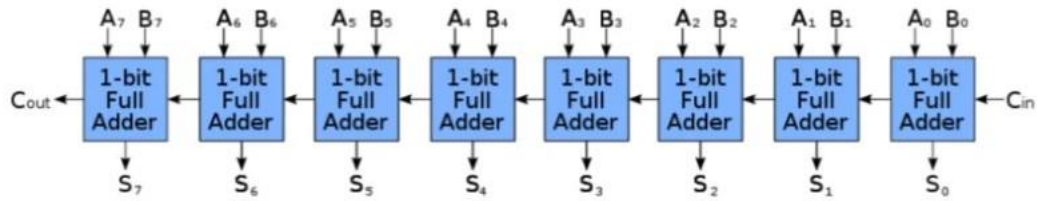


BLOCK DIAGRAM OF 8 BIT ADDER:




CODE FILE:

```
File Edit View Project Source Process Window Help
[Icons]
5 //
6 // Create Date: 17:01:06 09/19/2017
7 // Design Name:
8 // Module Name: b8FA
9 // Project Name:
10 // Target Devices:
11 // Tool versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21 module b8FA{
22     input [7:0] a,
23     input [7:0] b,
24     input cin,
25     output reg [7:0] sum,
26     output reg cout
27 };
28 always@ (a,b,cin)
29 (cout,sum)=a+b+cin;
30
31 endmodule
32
```

TEST BENCH CODE:

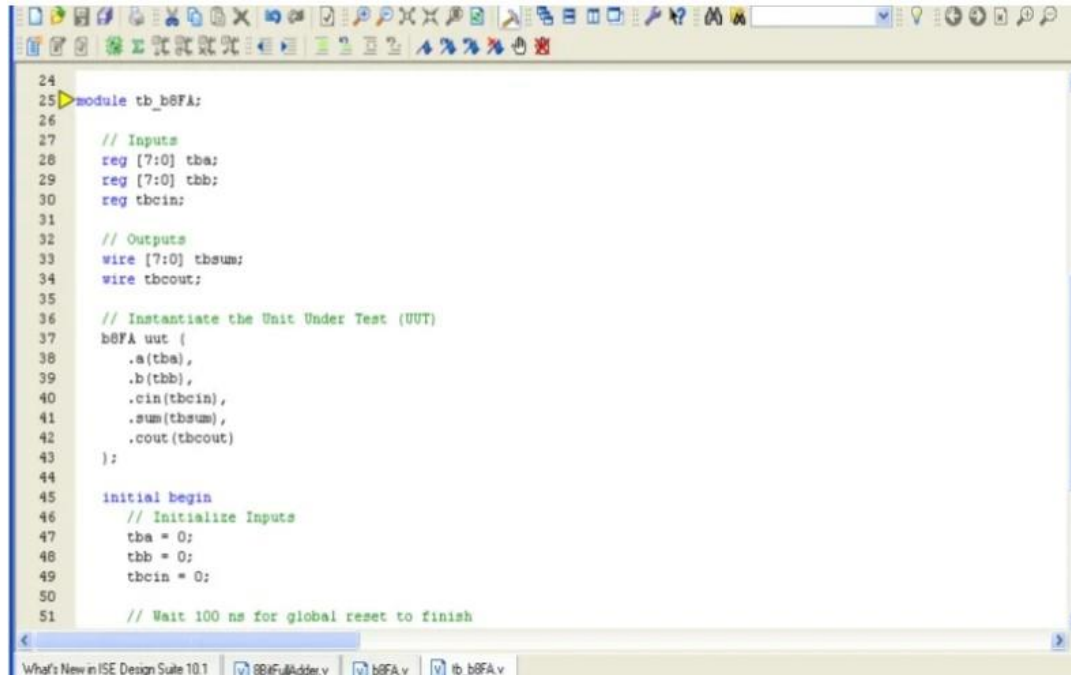
We design a Test Bench code to check our code's simulated functional behavior and also we put our initial value in test bench and also we put a value which we want to add.



```
24
25 module tb_8bFA:
26
27     // Inputs
28     reg [7:0] tba;
29     reg [7:0] tbb;
30     reg tbcin;
31
32     // Outputs
33     wire [7:0] tbsum;
34     wire tbcout;
35
36     // Instantiate the Unit Under Test (UUT)
37     b8FA uut (
38         .a(tba),
39         .b(tbb),
40         .cin(tbcin),
41         .sum(tbsum),
42         .cout(tbcout)
43     );
44
45     initial begin
46         // Initialize Inputs
47         tba = 0;
48         tbb = 0;
49         tbcin = 0;
50
51         // Wait 100 ns for global reset to finish
52     end
```

MORE SCREEN SHOT (tb_8bitFA):

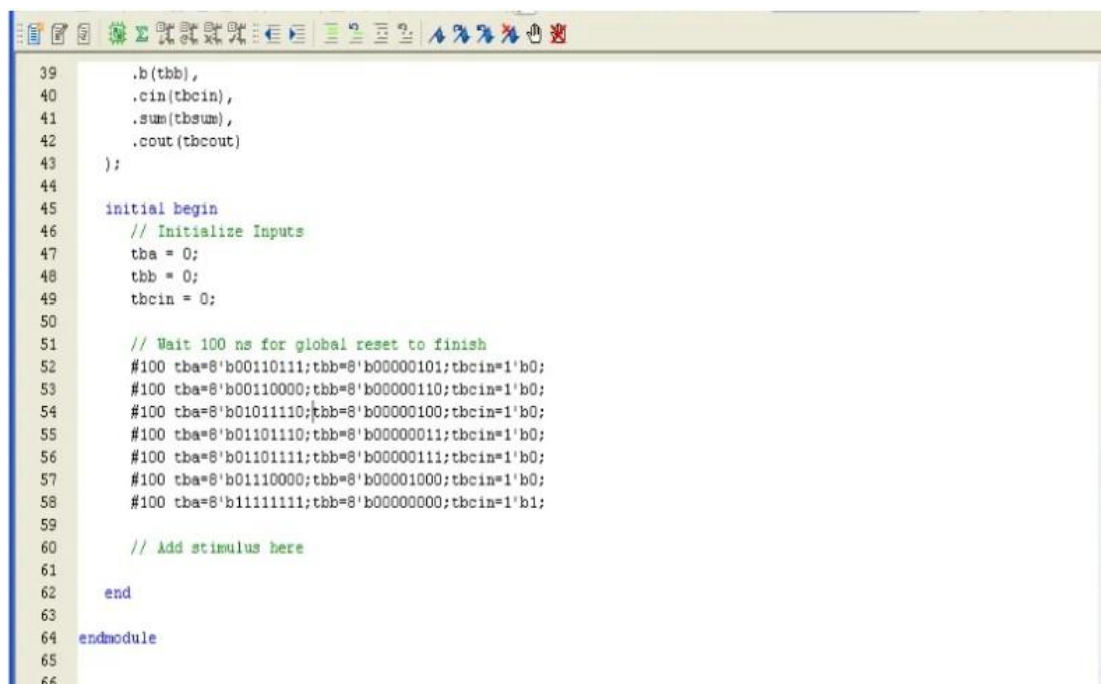Here we give input with **100ns** delay and also check the simulated result in the next screen shots.




```
39     .b(tbb),
40     .cin(tbcin),
41     .sum(tbsum),
42     .cout(tbcout)
43 );
44
45 initial begin
46     // Initialize Inputs
47     tba = 0;
48     tbb = 0;
49     tbcin = 0;
50
51     // Wait 100 ns for global reset to finish
52     #100 tba=8'b00110111;tbb=8'b00000101;tbcin=1'b0;
53     #100 tba=8'b00110000;tbb=8'b00000110;tbcin=1'b0;
54     #100 tba=8'b01011110;tbb=8'b00000100;tbcin=1'b0;
55     #100 tba=8'b01101110;tbb=8'b00000011;tbcin=1'b0;
56     #100 tba=8'b01101111;tbb=8'b00000111;tbcin=1'b0;
57     #100 tba=8'b01110000;tbb=8'b00001000;tbcin=1'b0;
58     #100 tba=8'b11111111;tbb=8'b00000000;tbcin=1'b1;
59
60     // Add stimulus here
61
62 end
63
64 endmodule
65
66
```

SIMULATED RESULT:


- **DECIMAL RESULT:**

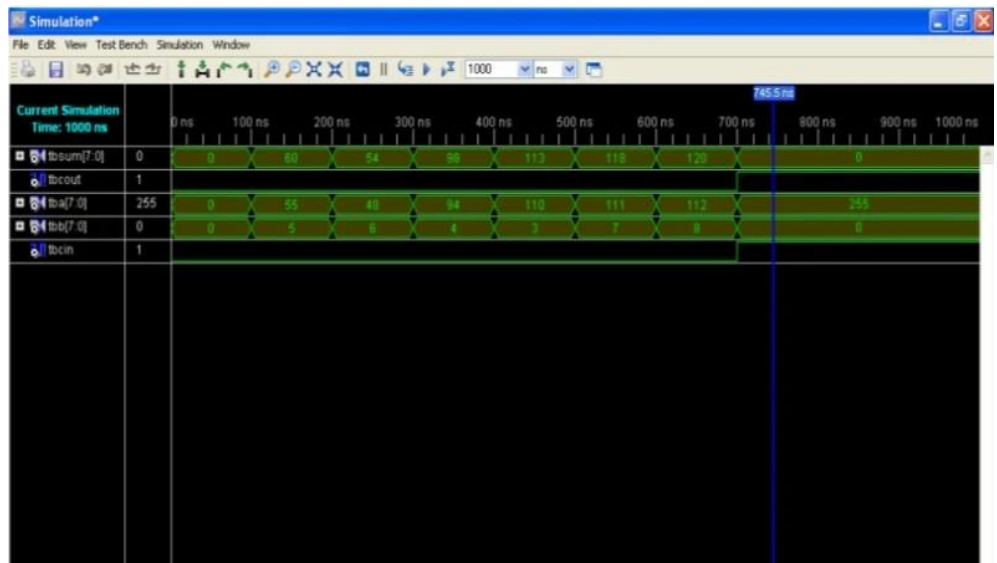Here we check the simulated result which is in decimal and also we can see clearly a carry result and also with **100ns** delay.



- **BINARY RESULT:**

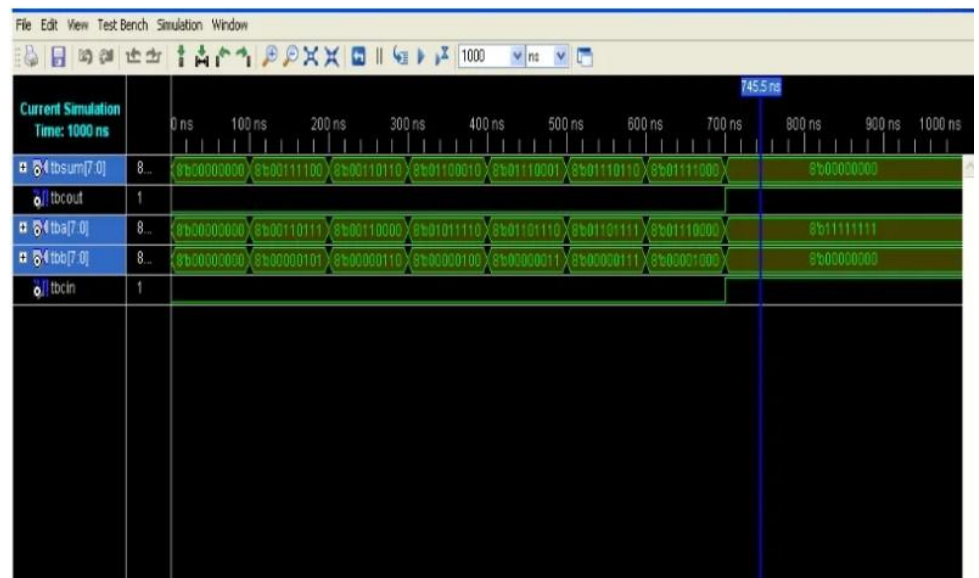We also check the result in binary by right click and selecting a binary instead of decimal. So, we get a simulated result in binary form.



Q: Why sum is zero when we add 1 in 255?

REASON:

As maximum bits show in 8'bit system is $255 = (11111111)_2$ as with increment of 1 bit it become 9'bit number $256 = (100000000)_2$ so we get MSB as carry **1** and remaining 8'bits as zeros.